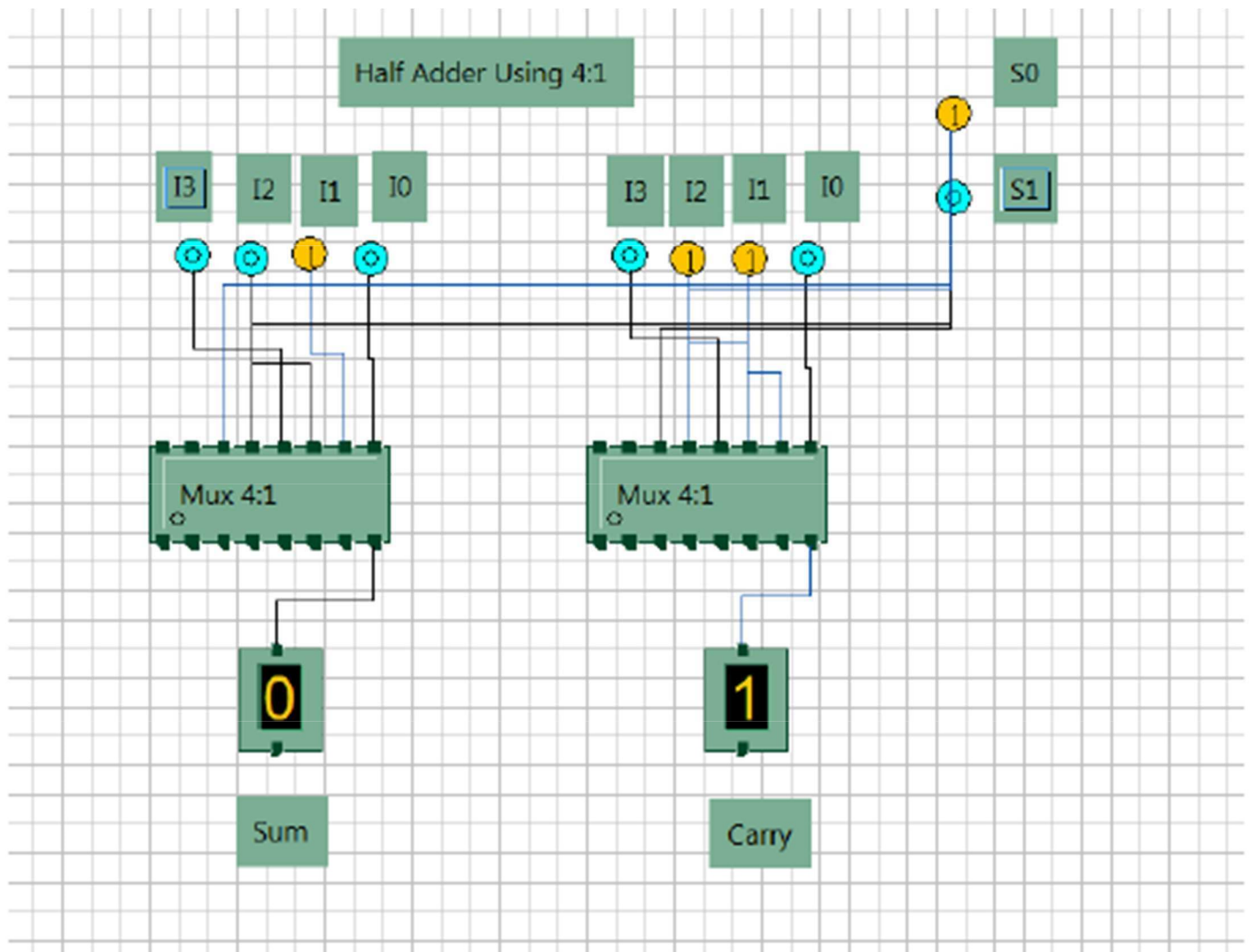



Experiment No.: 04

Kunj Hiteshbhai Trivedi

SE-9 Roll No.:38


Half Adder Using 4:1 Multiplexer



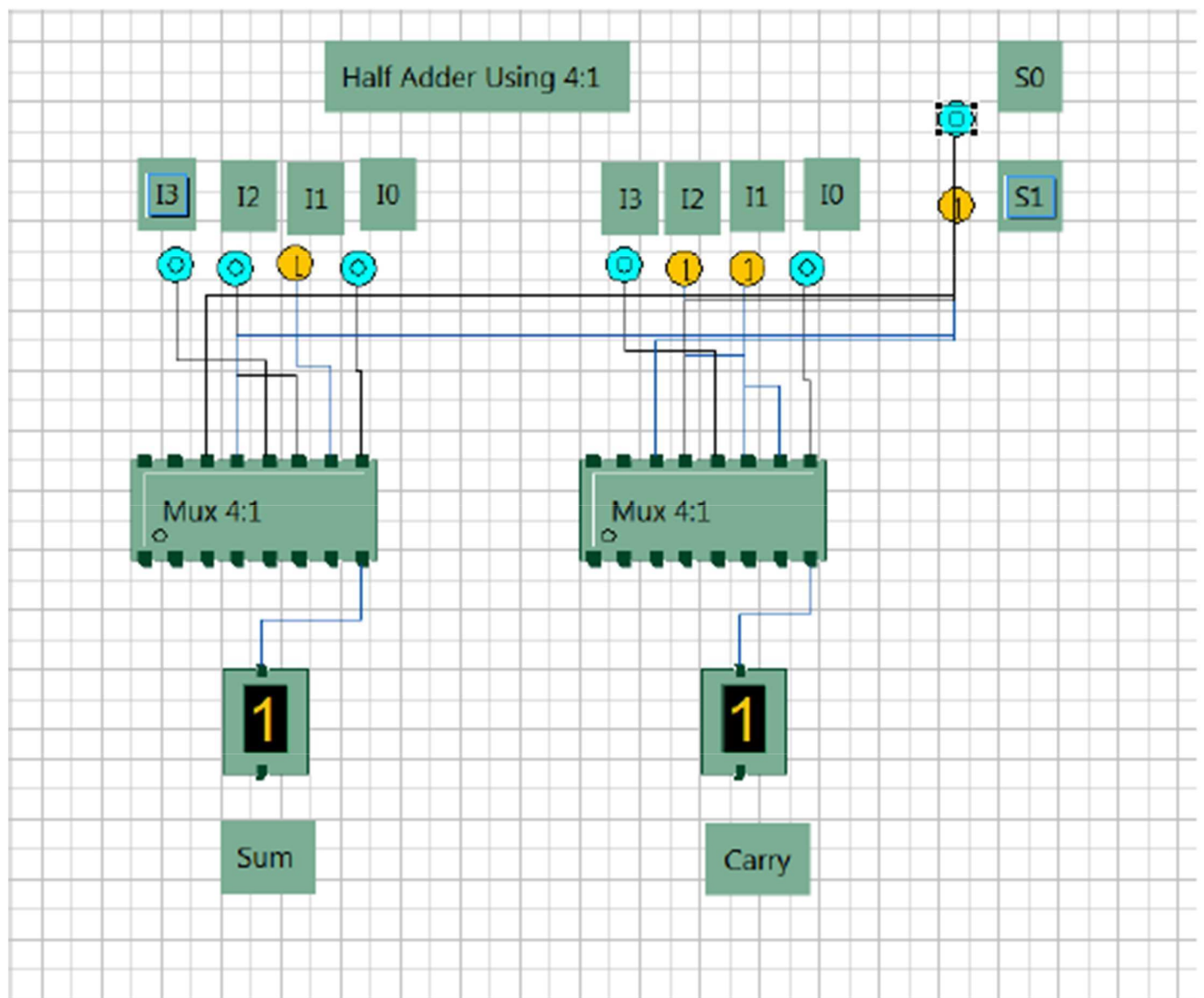

HALF SUBTRACTOR USING 4:1 MULTIPLEXER

Half Subtractor Using 4:1

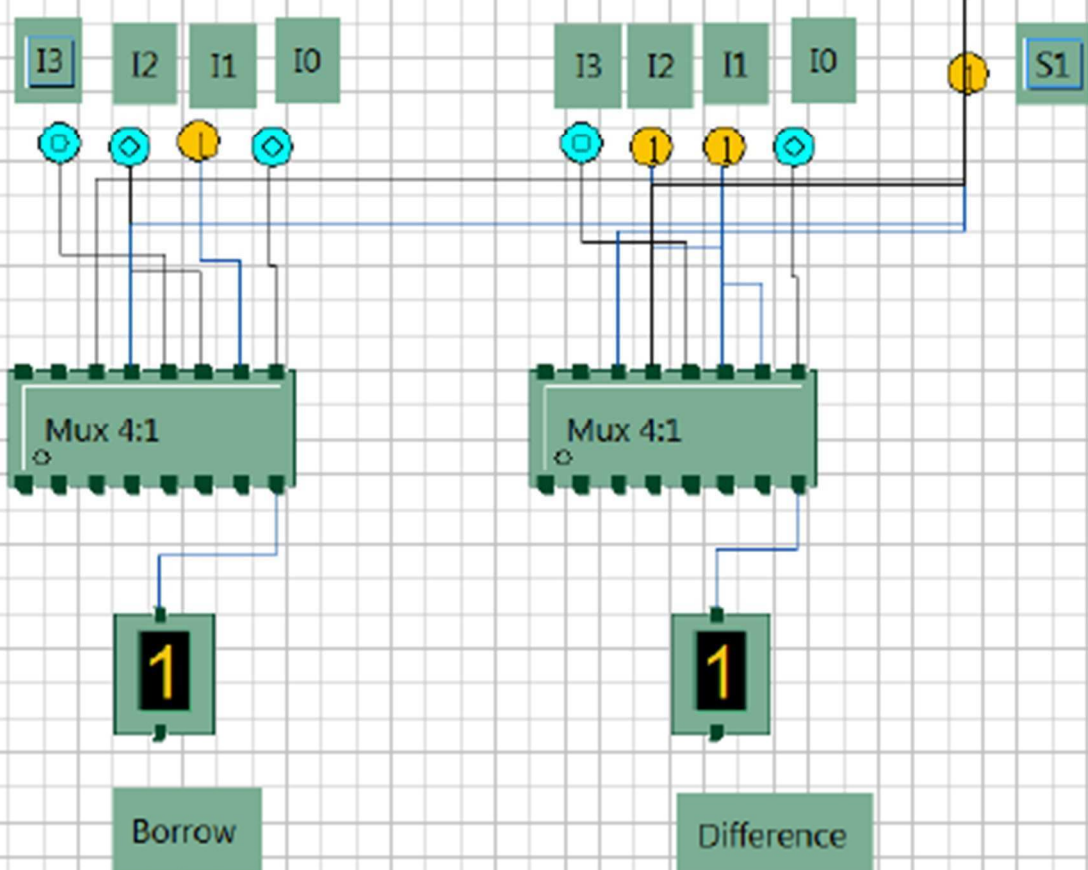

Half Subtractor Using 4:1

